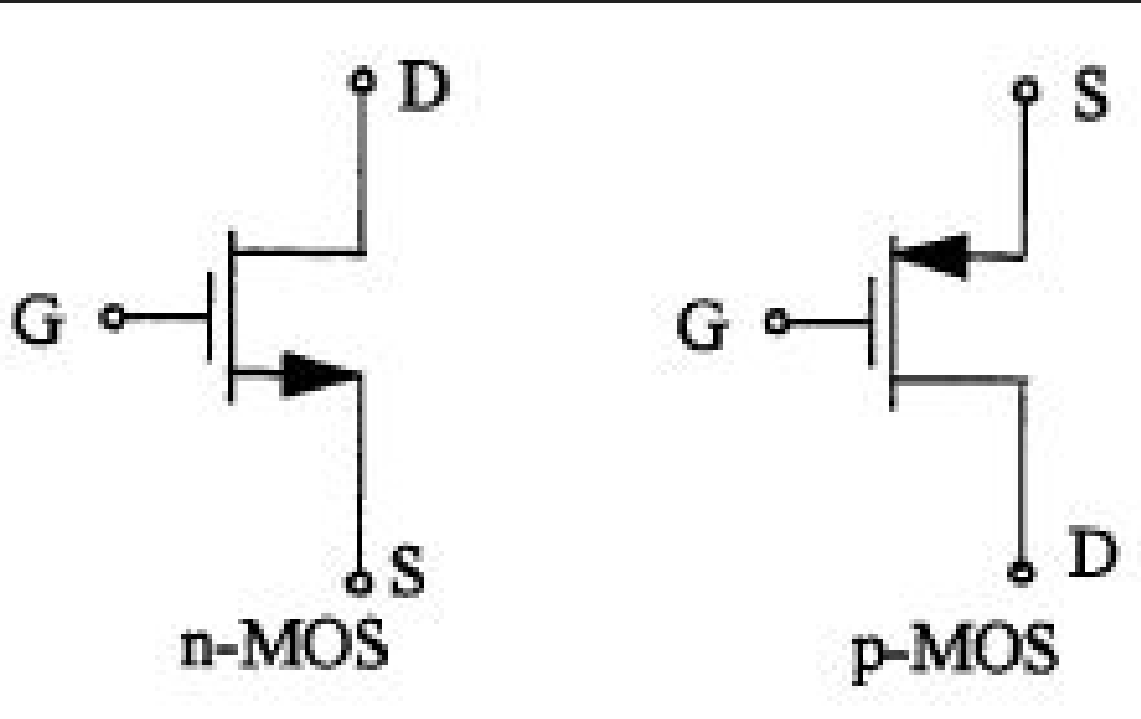


HKN ECE 342 Review Session 2

Anthony Li
Alec Wasowicz
Rex Geng


MOSFET's



MOSFET Operating Point

- Three regions of operation:
- Cutoff ($V_G < V_T$): $I_D = 0$
- Linear/Triode ($V_G > V_T$, $V_{DS} < V_{GS} - V_T$): $I_D = \mu_{n/p} C_{ox} (W/L) ((V_{GS} - V_T)V_{DS} - V_{DS}^2/2)$
- Saturation ($V_G > V_T$, $V_{DS} > V_{GS} - V_T$), $I_D = \mu_{n/p} C_{ox} (W/L) (1/2)(V_{GS} - V_T)^2$

MOSFET Incremental Model

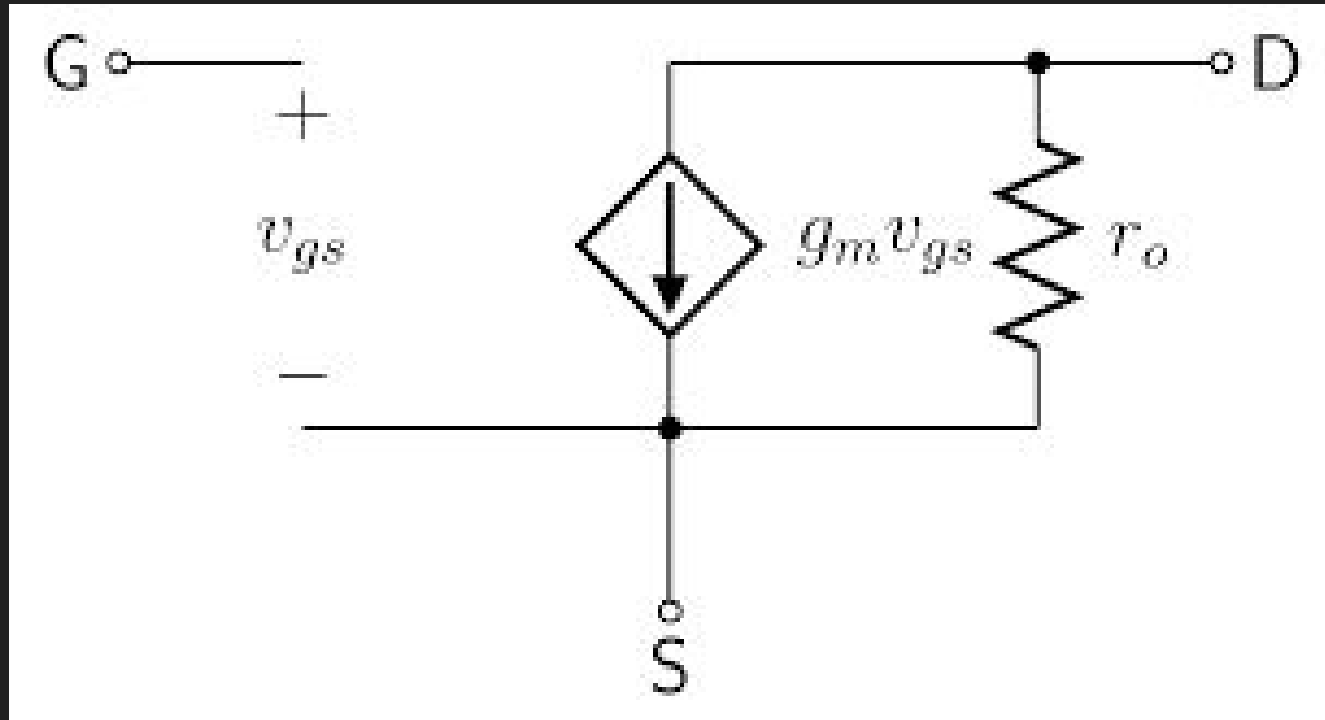

Gain Calculation


$$A_v = -G_M R_{out}$$

G_M = Small signal transconductance, ratio of i_{out} to v_{in}

R_{OUT} = Equivalent incremental output resistance

Common Amplifier Topologies

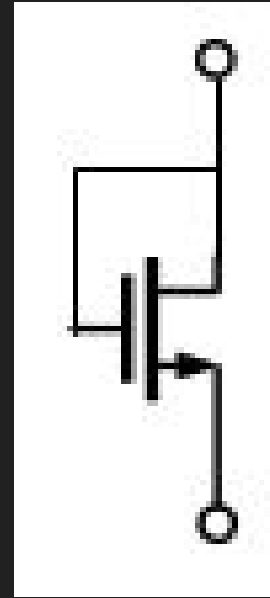1. Diode-tied Transistor
 - a. What is overdrive voltage here?
 - b. Is this always in saturation?
2. Common Source/Drain/Gate
 - a. Purpose of each topology?
 - b. equations
3. Common Source with Degeneration
4. Common Drain with Modulation
5. Cascode




1. Diode Tied Transistor

Common Source/Drain/Gate


$$R_{OUT} = R_D \parallel r_{ds}$$

$$G_m = g_m$$

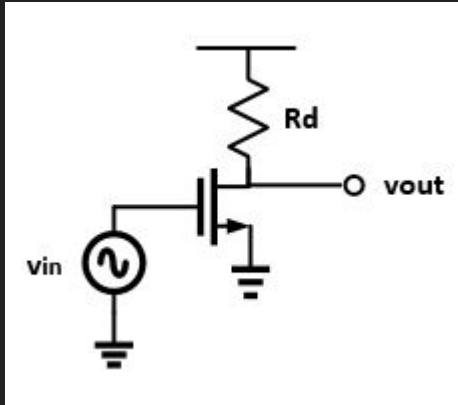


$$R_{OUT} = R_S \parallel (r_{ds} \parallel 1/g_m)$$

$$G_m = -g_m$$

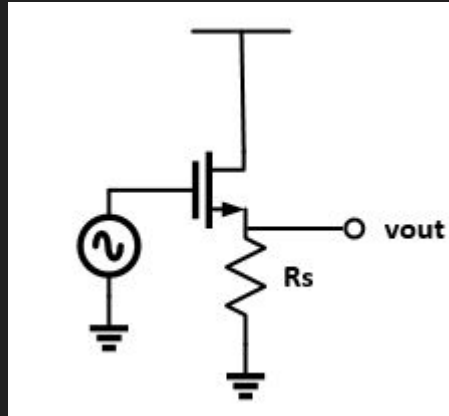


$$R_{OUT} = R_D \parallel r_{ds}$$

$$G_m = -g_m$$

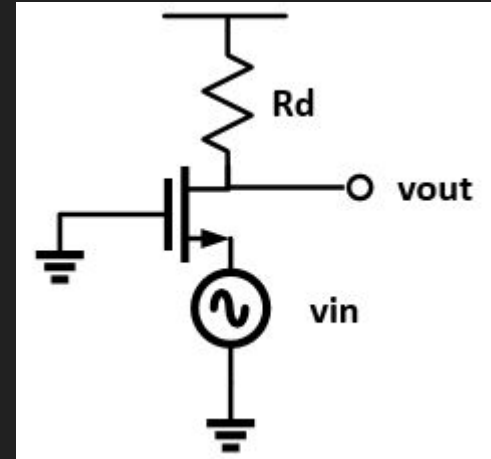

Degeneration

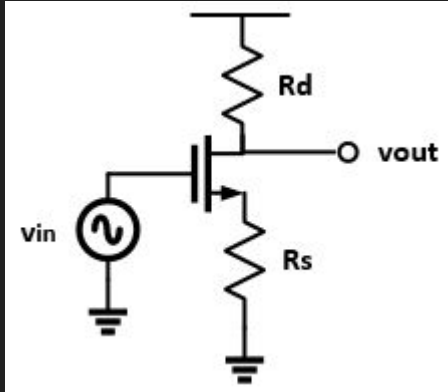
When a resistance is “viewed” through the drain, it appears bigger by a factor related to the transconductance.



$$R_{eq} = r_{ds} + R_S + g_m r_{ds} R_S$$

Degeneration Example

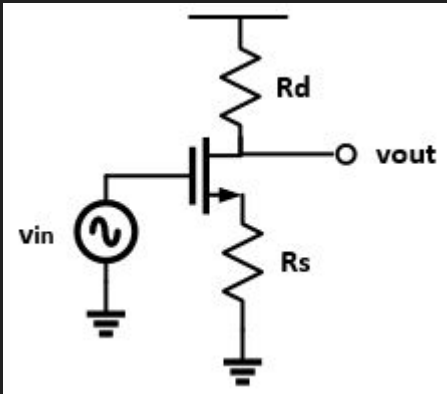Most common circuit with degeneration is a common source with a source resistance.




$$R_{OUT} = R_D \parallel (r_{ds} + R_S + g_m r_{ds} R_S)$$

$$G_m = g_m / (1 + g_m R_s)$$

Modulation


Resistances seen through the source seem smaller. Consider R_{in} from below:

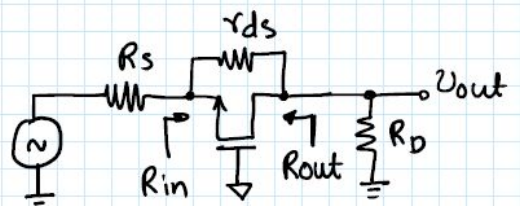
$$R_{in} = \frac{r_{ds} + R_D}{1 + g'_m r_{ds}} \approx \frac{1}{g'_m} + \frac{R_D}{g'_m r_{ds}}$$
$$= R_{in}|_{R_D=0} + \frac{R_D}{g'_m r_{ds}}$$

⇒ Resistance at the drain, R_D , appears $g'_m r_{ds}$ times **smaller** when looked from the source

$$R_{IN} = R_S + 1/g_m (1 + R_S/r_{ds}) \text{ for } g_m r_{ds} \gg 1$$

Modulation Example

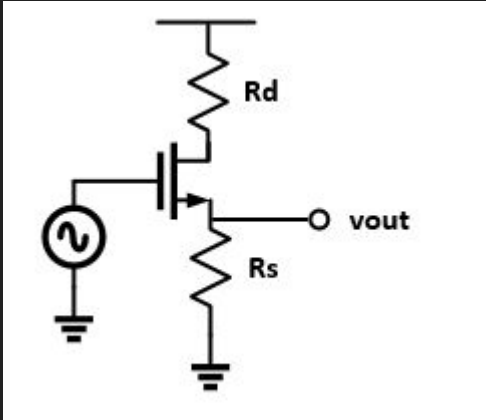

Cascode

