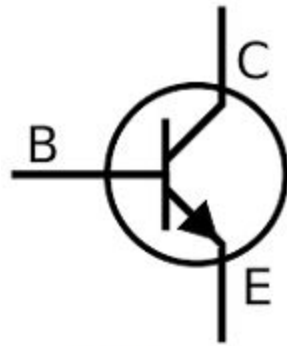


HKN ECE 342 Review


Session 3

Anthony Li
Rex Geng
Sergio Silva

BJT's



**NPN
Bipolar Junction
Transistor**

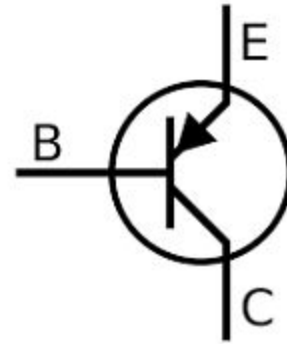


**PNP
Bipolar Junction
Transistor**

BJT Operating Point

- Three regions of operation:
- Cutoff
- Saturation
- Forward Active
 - $V_T = kt/q$
 - $I_C = \beta I_B$
 - $I_E = I_C + I_B$
 - $\beta = g_m R_x$

BJT Incremental Model

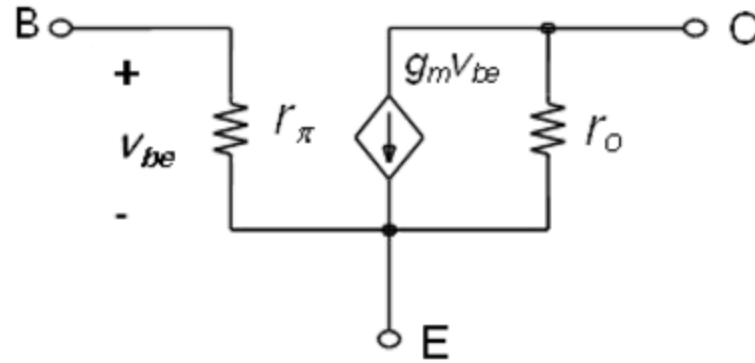

Gain Calculation

$$A_v = -G_M R_{out}$$

G_M = Small signal transconductance, ratio of i_{out} to v_{in}

R_{OUT} = Equivalent incremental output resistance

R_{IN} = Equivalent incremental input resistance

Common Amplifier Topologies

1. Diode-tied Transistor
 - a. What is overdrive voltage here?
 - b. Is this always in saturation?
2. Common Emitter/Collector/Gate
 - a. Purpose of each topology?
 - b. equations
3. Common Emitter with Degeneration
4. Common Collector with Modulation
5. Cascode



Terminal Impedances of BJT's

$$R_C = r_o$$

$$R_B = R_{\pi}$$

$$R_E = R_{\pi}/(\beta + 1)$$
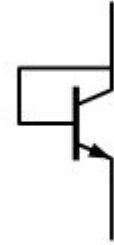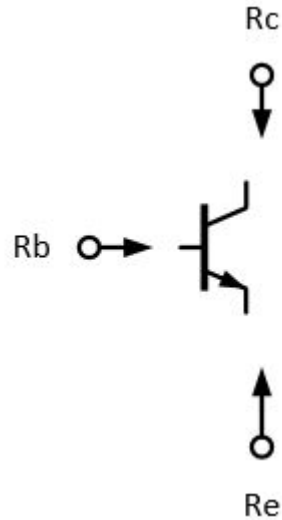
$$\text{Diode-Tied} = R_{\pi}/(\beta + 1)$$




1. Diode Tied Transistor

Common Emitter/Collector/Base

$$R_{OUT} = R_c \parallel r_o$$

$$R_{IN} = R_\pi + R_B$$


$$G_m = \beta / (R_\pi + R_B)$$

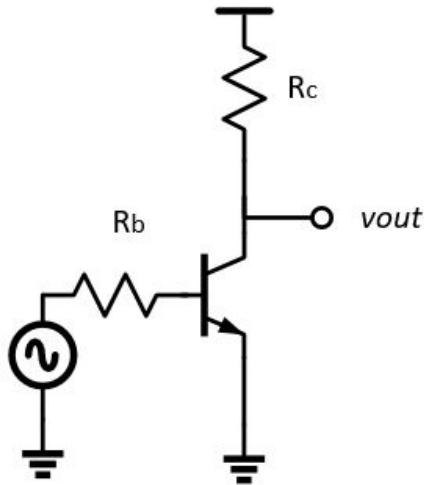

$$R_{OUT} = ((R_\pi + R_B) / (\beta + 1)) \parallel R_E$$

$$R_{IN} = R_B + R_\pi + ((\beta + 1)) R_E$$


$$G_m = -(\beta + 1) / (R_\pi + R_B)$$

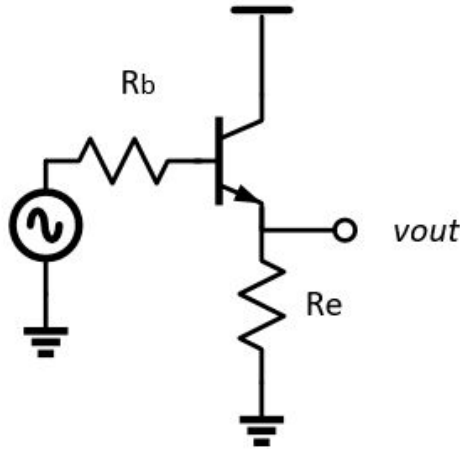

$$R_{OUT} = R_c \parallel r_o$$


$$R_{IN} = (R_\pi + R_B) / (\beta + 1)$$

$$G_m = \beta / (R_\pi + R_B)$$

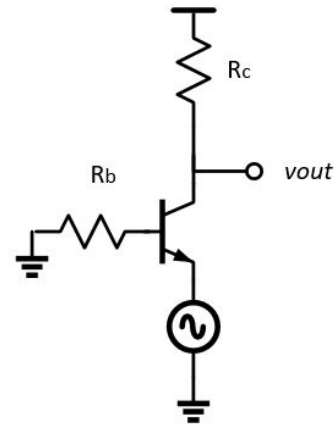

Degeneration

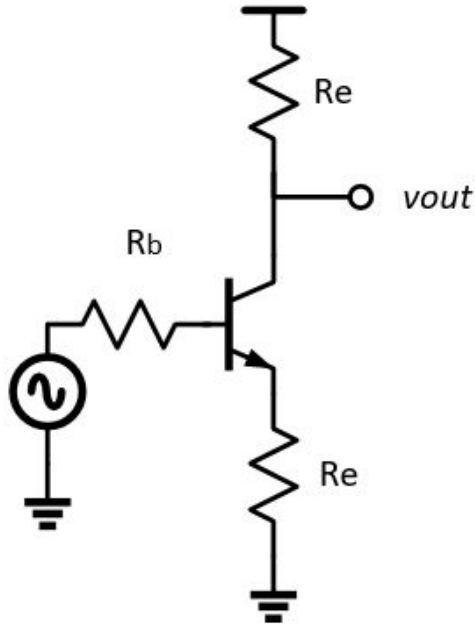When a resistance is “viewed” through the collector, it appears bigger by a factor related to the transconductance.




$$G_m = 1 / \left(\frac{R_B + R_{\pi}}{\beta} + \left(\frac{\beta + 1}{\beta} \right) R_E \right)$$

$$R_{IN} = R_B + R_{\pi} + (\beta + 1) R_E$$

Modulation

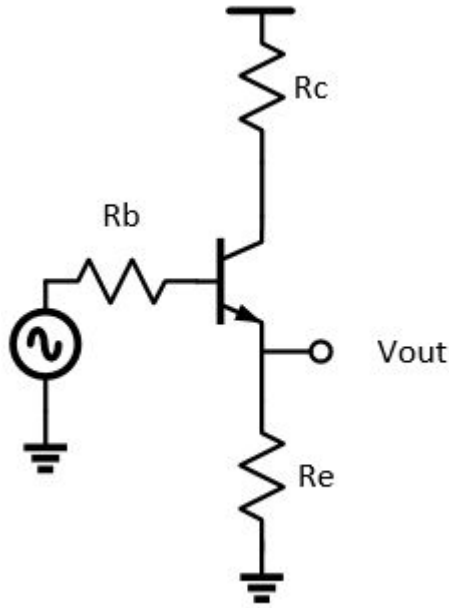
Resistances seen through the Emitter seem smaller.



$$G_m = -(\beta + 1) / (R_B + R_{\pi})$$

$$R_{IN} = R_B + R_{\pi} + ((\beta + 1))R_E$$

Cascode

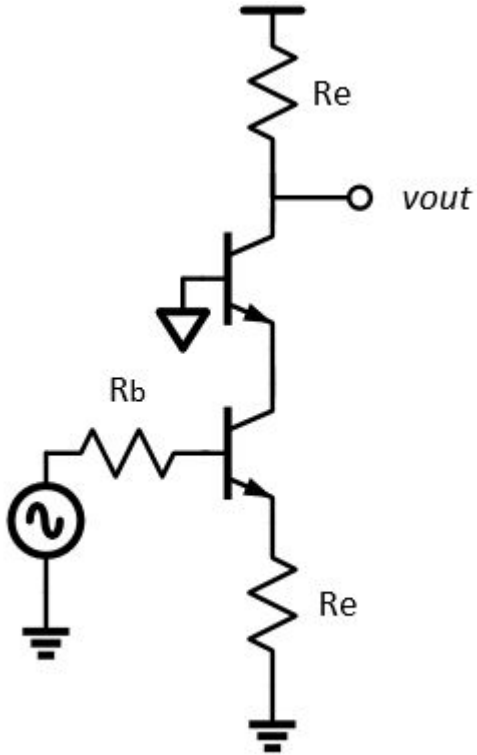

Bode Plots

Magnitude

Pole: Roll down by 20 db/dec, 6 db/oct

Zero: Roll up by 20 db/dec, 6 db/oct

Phase: $\arctan(\omega/\omega_p)$

Usually -90° for poles, $+90^\circ$ for zeros

$\omega_{ugf} = 20\log|A_n| * \omega_{pn}$ where n is the pole located before unity gain frequency