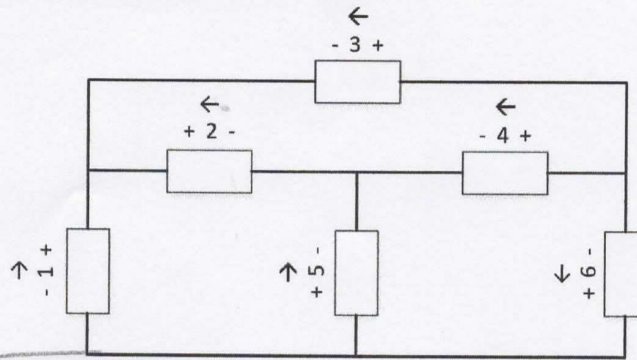


ECE 110 Exam 1 Review Session Worksheet

1. Given that $V_1 = -9V$, $V_3 = 5V$, $V_4 = -6V$ and $I_2 = -2A$, $I_3 = 5A$, $I_6 = -7A$, find the remaining unknown voltages and currents, and power for each component. Be careful of signs!



	I	V	P
#1	-3	-9	$-IV \rightarrow -27W$
#2	-2	-11	$-IV \rightarrow -22W$
#3	5	5	$+IV \rightarrow 25W$
#4	2	-6	$+IV \rightarrow -12W$
#5	-4	-2	$+IV \rightarrow 8W$
#6	-7	4	$-IV \rightarrow 28W$

$$I_1 + I_2 + I_3 = 0 \rightarrow I_1 = -3A$$

$$I_3 + I_4 + I_5 = 0 \rightarrow I_4 = 2A$$

$$I_2 = I_5 + I_4 \rightarrow I_5 = -4A$$

$$V_1 + V_3 + V_6 = 0 \rightarrow V_6 = 4V$$

$$V_5 = V_4 + V_6 \rightarrow V_5 = -2V$$

$$V_1 + V_5 = V_2 \rightarrow V_2 = -11V$$

2. Given that $V_1 = 1V$, $V_2 = -6V$, $V_3 = 7V$, $V_4 = -2V$, and $R = 10\Omega$, determine V_{AB} , V_{BC} , and I .

KVL for V_{AB}


$$\sum V_{rises} = \sum V_{drops}$$

$$V_1 + V_4 = V_2 + V_{AB} + V_3$$

$$V_{AB} = -2V$$

$$I = \frac{V_{AB}}{R} = \frac{-2V}{10\Omega}$$

$$= -0.2A$$

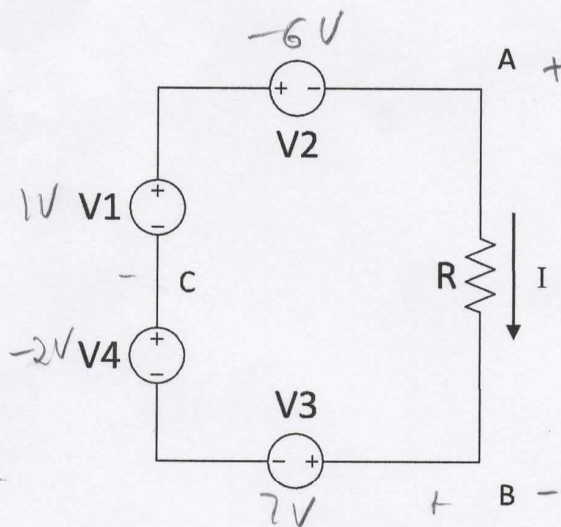

KVL for V_{BC}

$$\sum V_{rises} = \sum V_{drops}$$

$$V_1 = V_{BC} + V_2 + V_{AB}$$

$$V_{BC} = 9V$$

3. Consider a PWM waveform with duty cycle = 64%, peak-to-peak voltage = 5V, and frequency = 20kHz.
- What is the V_{rms} of this PWM waveform?
 - Suppose we know that this PWM can deliver an average power of 0.25W to an unknown resistor. What is the resistance of this unknown resistor?
 - Suppose we want to generate a sinusoidal waveform that provides the same average power at the same frequency. What should be the amplitude of this sinusoid?
 - Do the sinusoid and PWM waveform deliver the same amount of power to the resistor?

$$a) V_{rms} = 5\sqrt{0.64} = 4V$$

$$b) P_{avg} = \frac{V_{rms}^2}{R} \rightarrow R = \frac{V_{rms}^2}{P_{avg}} = \frac{16V^2}{0.25W} = 64\Omega$$

$$c) V_{rms}^2 = P_{avg}R \quad V_{rms} = \sqrt{P_{avg}R} = 4V \quad V_{rms} = \frac{A}{\sqrt{2}} \quad A = V_{rms}\sqrt{2}$$

$$A = 4\sqrt{2}$$



d) Yes!

4. Find the I-V Characteristic of the following circuit. Be careful of the direction of I!

$$V_{oc} = 5 \cdot 8 = 40V$$

$$I_{sc} = 5 \left(\frac{8}{10} \right) = 4A$$

↳ y-intercept = -4

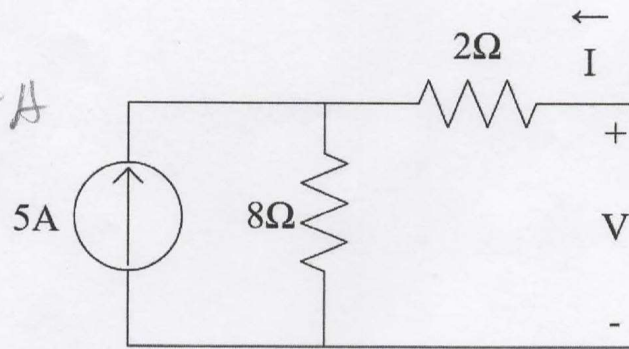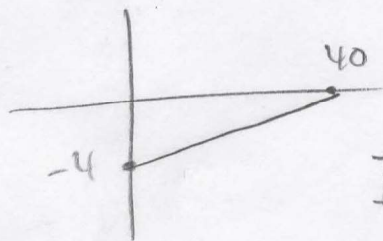

$$I = mV + b$$

$$b = -4$$

$$m = \frac{4}{40} = \frac{1}{10}$$

$$I = \frac{1}{10}V - 4$$

5. Compute the power of each of the following elements.

$$P_R = \frac{V^2}{R} = \frac{8^2}{4} = 16W$$

$$P_I = -IV = 24W$$

$$P_V = -40W$$

$$\rightarrow \Sigma P = 0$$

